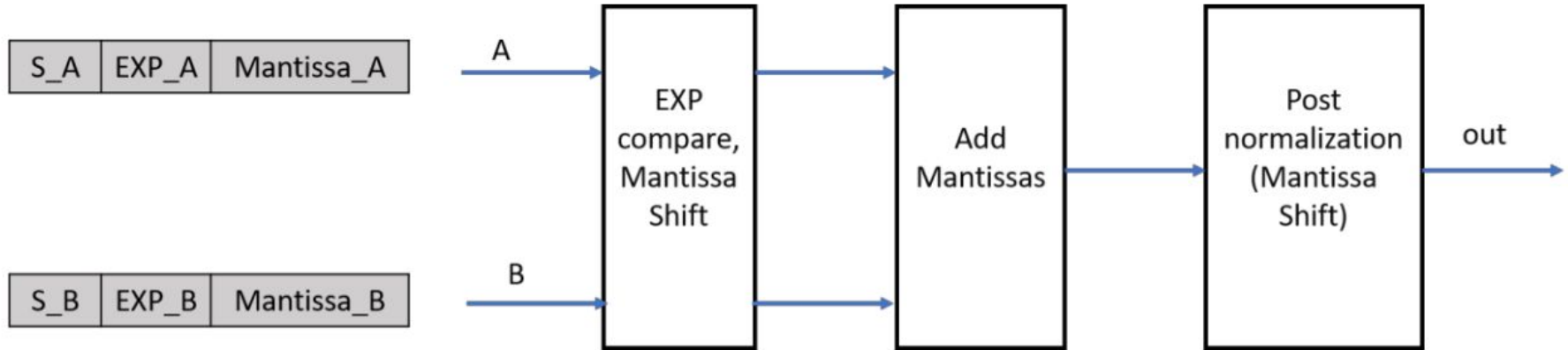


Embedded Systems (ECE340)

Project 1

Χριστόδουλος Ζερδαλής & Τσιαντός Δημήτριος
(3531 & 3796)

Step 1: Design



Step 1: Example

A: 1 10000101 101111010000000000000000 (-111.25)

B: 0 10001010 001010101011110000000000 (2389.875)


$\text{expA} - \text{expB} = 138 - 133 = 5$ (0 αν η διαφορά ≥ 24)

$\text{mantissa A} \gg 5 = 000011011110100000000000$


$\text{mantissa A} + \text{mantissa B} = 0.0000110111101 + 1.00101010101111$
 $= 1.001110001010010000000000$

$A + B = 0 \ 10001010 \ 000111001101010000000000 = 2278.625$

Step 2: Pipelined Design

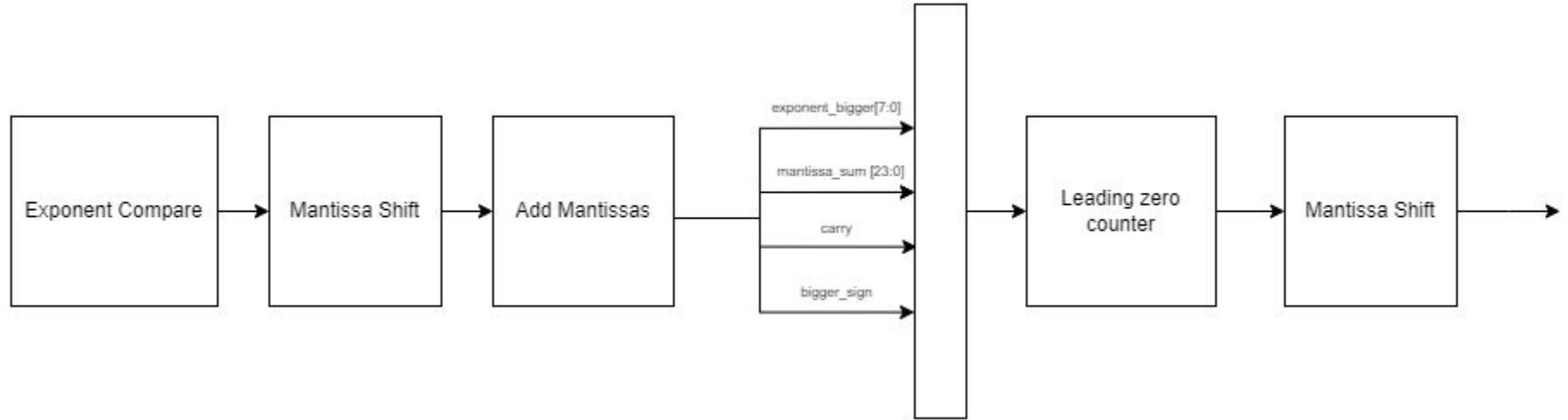

Step 3: Top diagram

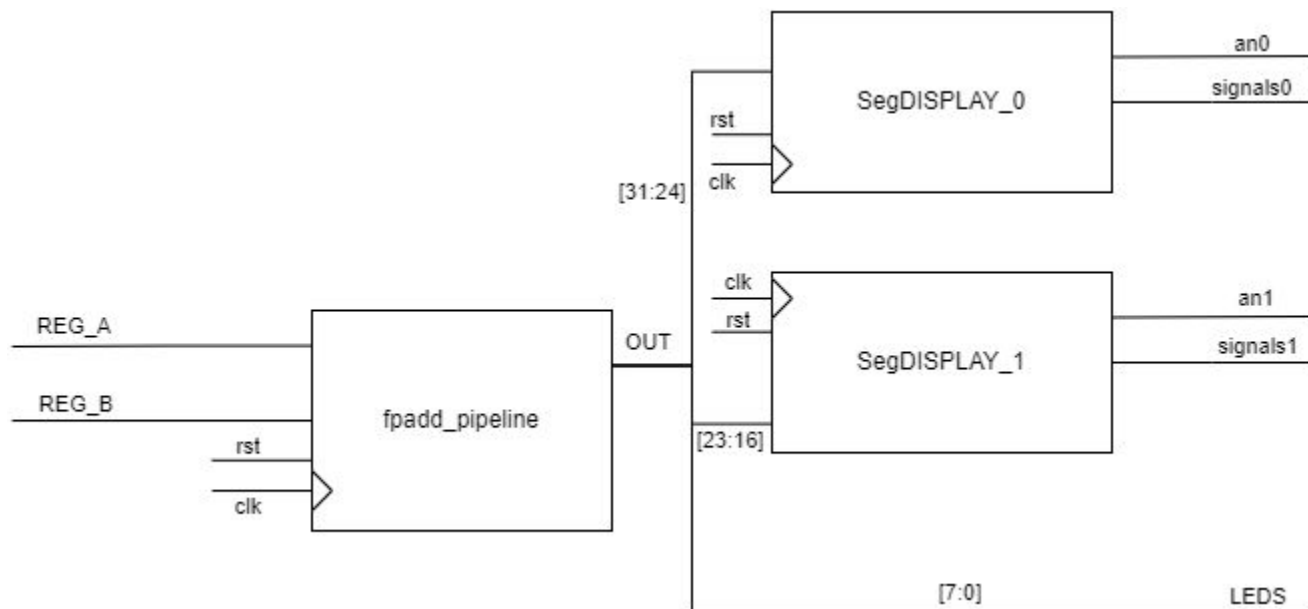

Step 3: Seven Segment Displays connections


Table 16 - Pmod Connections

Pmod	Signal Name	Zynq pin	Pmod	Signal Name	Zynq pin
JA1	JA1	Y11	JB1	JB1	W12
	JA2	AA11		JB2	W11
	JA3	Y10		JB3	V10
	JA4	AA9		JB4	W8
	JA7	AB11		JB7	V12
	JA8	AB10		JB8	W10
	JA9	AB9		JB9	V9
	JA10	AA8		JB10	V8


Pmod	Signal Name	Zynq pin	Pmod	Signal Name	Zynq pin
JC1 Differential	JC1_N	AB6	JD1 Differential	JD1_N	W7
	JC1_P	AB7		JD1_P	V7
	JC2_N	AA4		JD2_N	V4
	JC2_P	Y4		JD2_P	V5
	JC3_N	T6		JD3_N	W5
	JC3_P	R6		JD3_P	W6
	JC4_N	U4		JD4_N	U5
	JC4_P	T4		JD4_P	U6

Pmod	Signal Name	Zynq pin	MIO
JE1 MIO Pmod	JE1	A6	MIO13
	JE2	G7	MIO10
	JE3	B4	MIO11
	JE4	C5	MIO12
	JE7	G6	MIO0
	JE8	C4	MIO9
	JE9	B6	MIO14
	JE10	E6	MIO15


Step 4: Top diagram

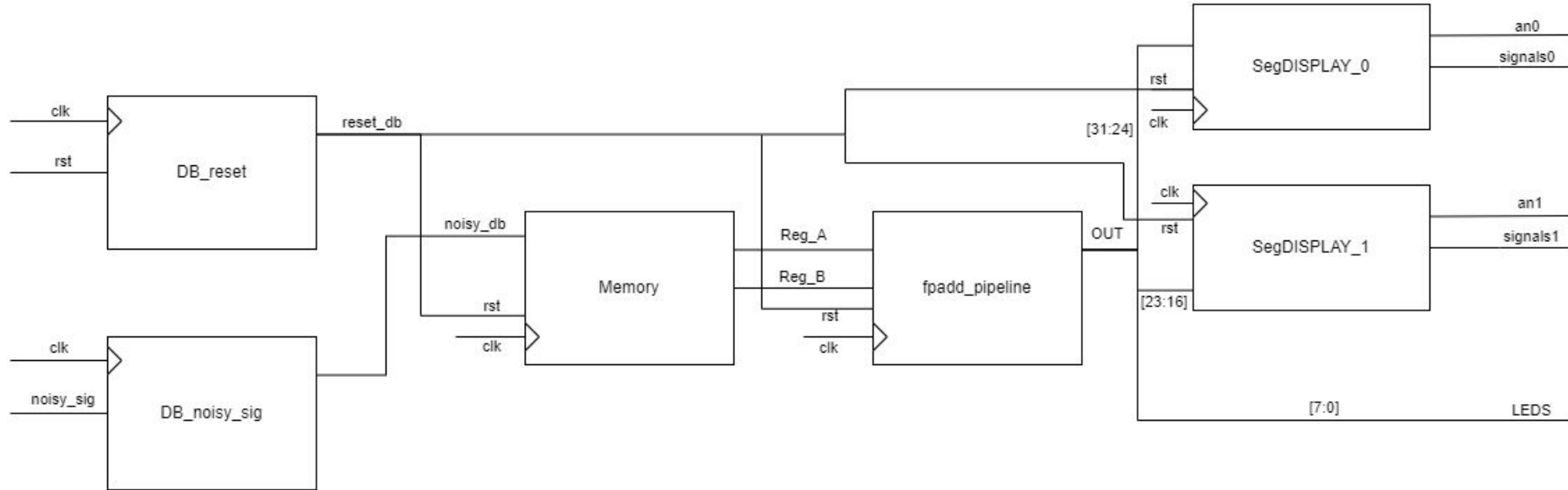


Step 4: FSM

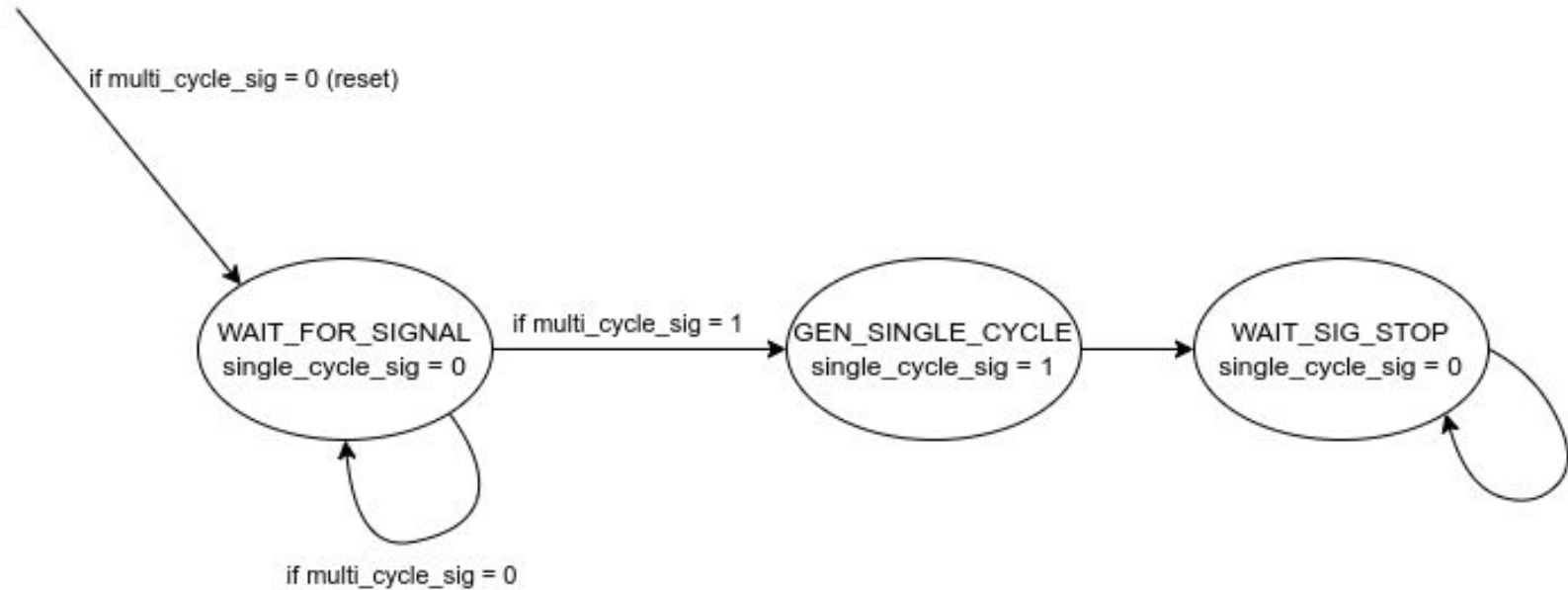


Step 4: Debounce

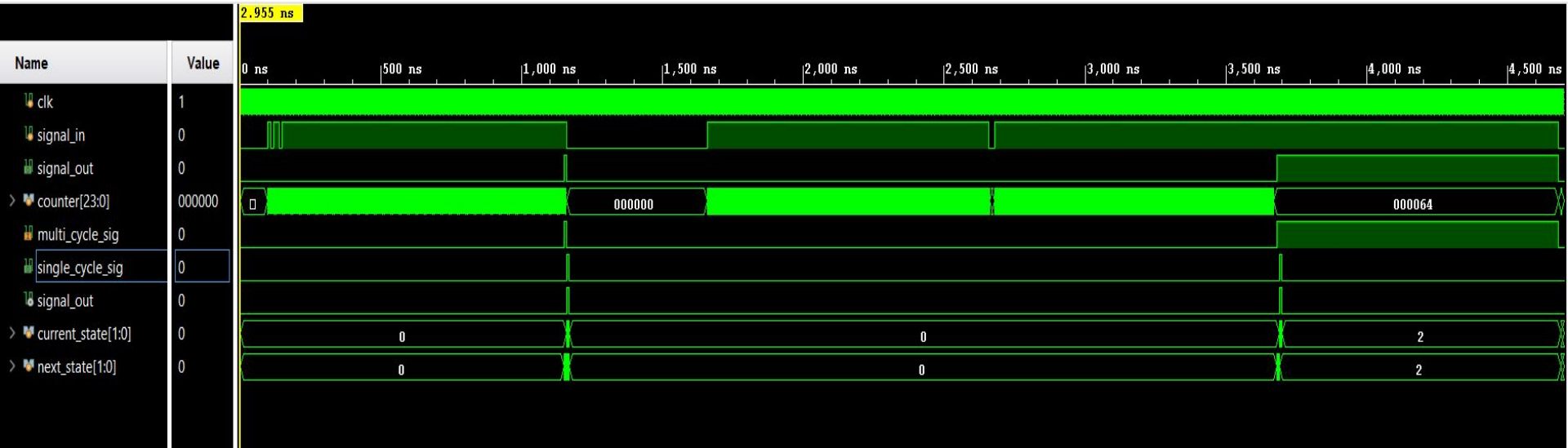


Step 4: Limit case 1

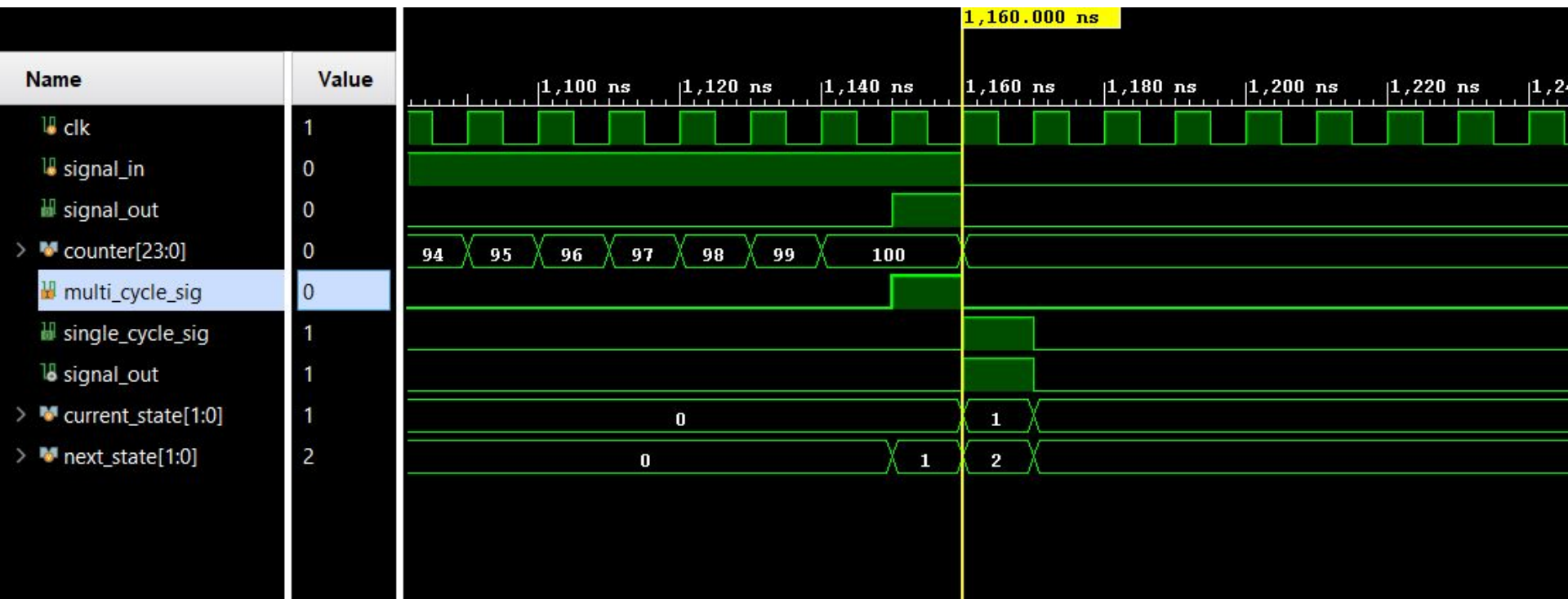

Step 4: Limit case 2

 

Step 4: behavioral sim

 

Step 4: Implementation sim

